

Experiment 4 - Universal Rotator

1. Design

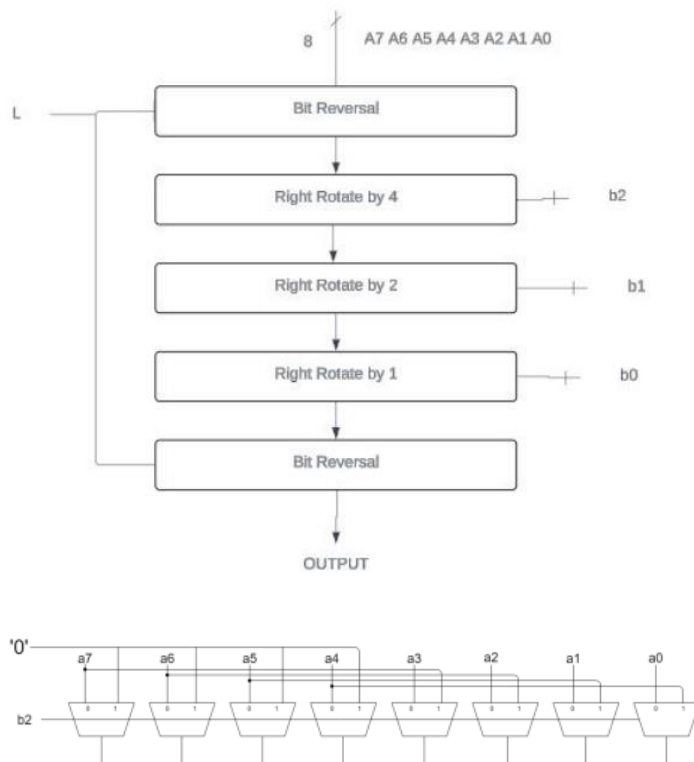


Figure 2: Right shift by 4 bits

Simulation

