

Lab 6 report

23b1269

Foram trivedi

Pen paper design



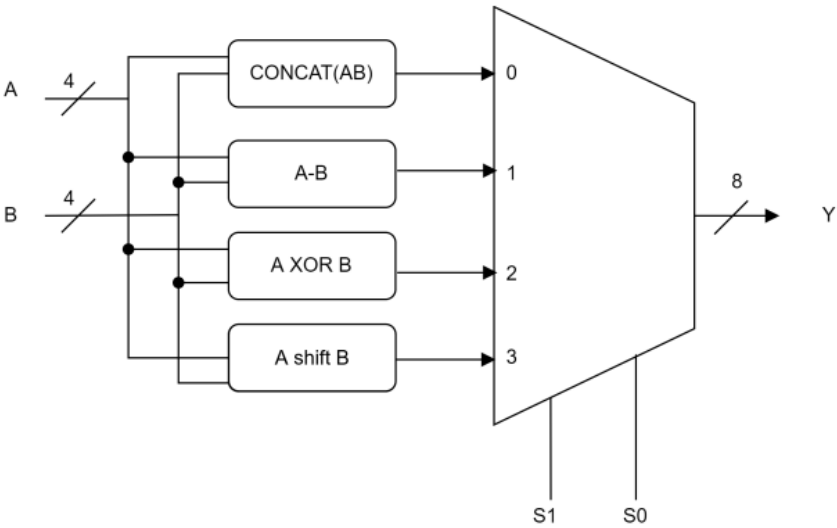
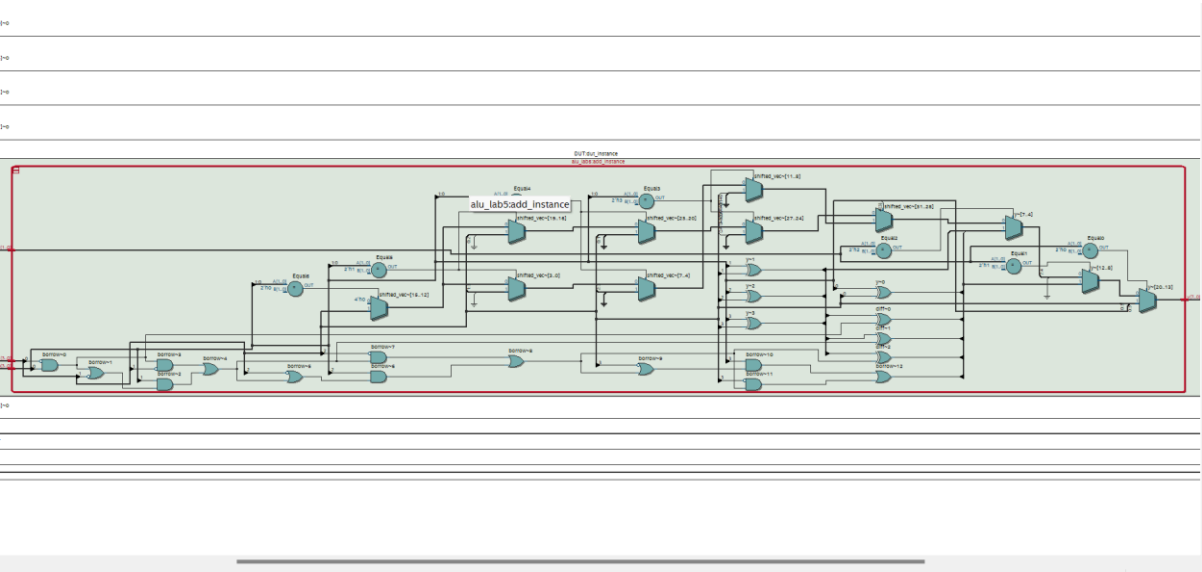


Figure 1: ALU with 4 functions

S1 S0	ALU Output
0 0	Concatenate two 4-bit inputs A and B
0 1	Performs A-B Operation
1 0	Performs A xor B Operation
1 1	Shift A by B bits [B3 - 0(left)/1(right)] [B2 - unused] [B1 B0 - no. of bits to be shifted]

Simulations

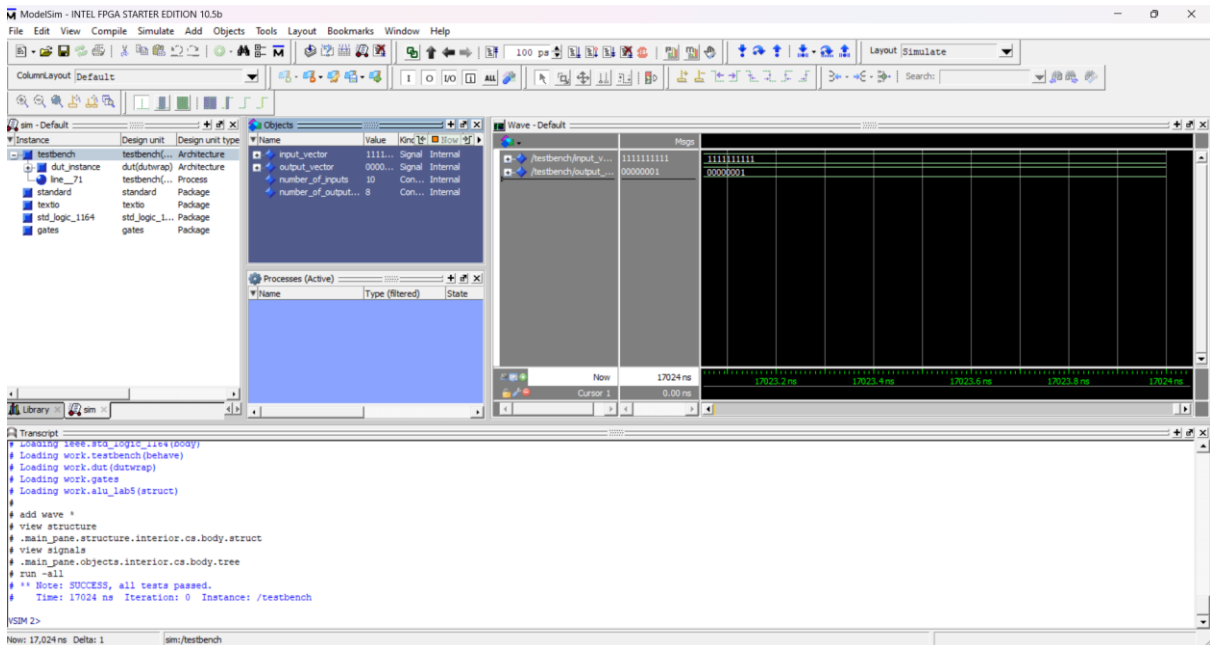

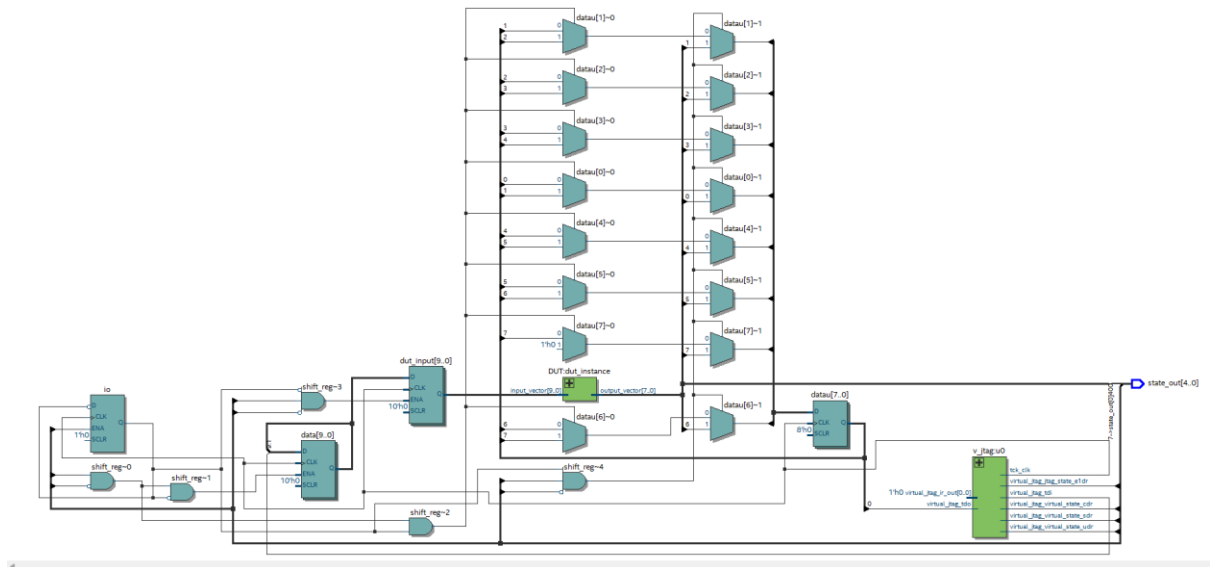

Scan chain output

0000000000	00000000	Success
0000000001	00000001	Success
0000000010	00000010	Success
0000000011	00000011	Success
0000000100	00000100	Success
0000000101	00000101	Success
0000000110	00000110	Success
0000000111	00000111	Success
0000001000	00001000	Success
0000001001	00001001	Success
0000001010	00001010	Success
0000001011	00001011	Success
0000001100	00001100	Success
0000001101	00001101	Success
0000001110	00001110	Success
0000001111	00001111	Success
0000010000	00010000	Success
0000010001	00010001	Success
0000010010	00010010	Success
0000010011	00010011	Success
0000010100	00010100	Success
0000010101	00010101	Success
0000010110	00010110	Success
0000010111	00010111	Success
0000011000	00011000	Success
0000011001	00011001	Success
0000011010	00011010	Success
0000011011	00011011	Success
0000011100	00011100	Success
0000011101	00011101	Success
0000011110	00011110	Success
0000011111	00011111	Success
0000100000	00100000	Success
0000100001	00100001	Success
0000100010	00100010	Success